
 



## Part A - simulation 1

 


## Part A - simulation 2



## Part A - simulation 3

 

## Part A - simulation 4

 


Truth Table for 4-bit Comparator

Comparison Inputs from 1-Bit Comparators												4-Bit Comparator Outputs		
A3<B3	A3=B3	A3>B3	A2<B2	A2=B2	A2>B2	A1<B1	A1=B1	A1>B1	A0<B0	A0=B0	A0>B0	A<B	A=B	A>B
0	0	1	X	X	X	X	X	X	X	X	X	0	0	1
1	0	0	X	X	X	X	X	X	X	X	X	1	0	0
0	1	0	0	0	1	X	X	X	X	X	X	0	0	1
0	1	0	1	0	0	X	X	X	X	X	X	1	0	0
0	1	0	0	0	0	0	0	1	X	X	X	0	0	1
0	1	0	0	0	0	1	0	0	X	X	X	1	0	0
0	1	0	0	0	0	0	0	0	0	0	1	0	0	1
0	1	0	0	0	0	0	0	0	1	0	0	1	0	0
0	1	0	0	1	0	0	1	0	0	1	0	0	1	0

Compilation Report

Flow Status	Successful - Sun Jun 18 19:01:32 2017
Quartus Prime Version	15.1.0 Build 185 10/21/2015 SJ Standard Edition
Revision Name	LogicalStep_Lab3_top
Top-level Entity Name	LogicalStep_Lab3_top
Family	MAX 10
Device	10M08SAE144C8Q
Timing Models	Final
Total logic elements	49 / 8,064 ( < 1 % )
Total combinational functions	49 / 8,064 ( < 1 % )
Dedicated logic registers	11 / 8,064 ( < 1 % )
Total registers	11
Total pins	30 / 101 ( 30 % )
Total virtual pins	0
Total memory bits	0 / 387,072 ( 0 % )
Embedded Multiplier 9-bit elements	0 / 48 ( 0 % )
Total PLLs	0 / 1 ( 0 % )
UFM blocks	0 / 1 ( 0 % )
ADC blocks	0 / 1 ( 0 % )

## RTL Viewer

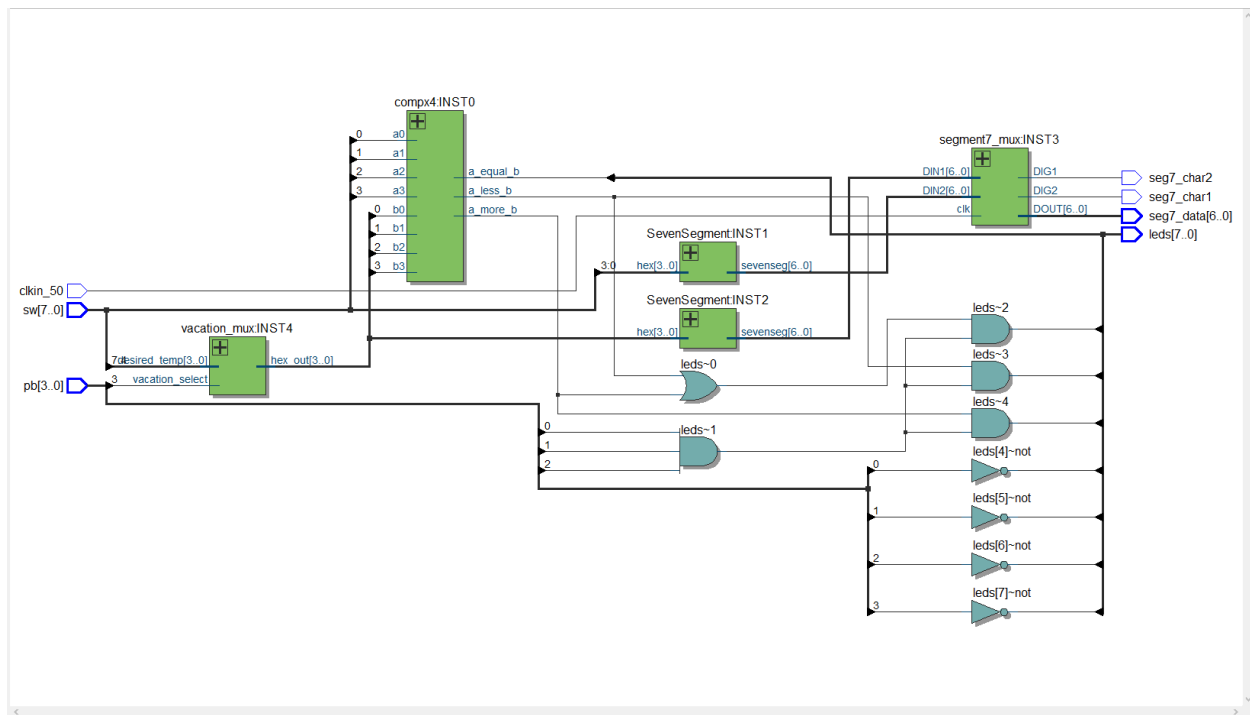

## Compx1

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity compx1 is
5  port (
6      bit_A, bit_B          : in std_logic; --one-bit input (A, B)
7      A_less_B, A_equal_B, A_more_B : out std_logic --one-bit output
8  );
9
10 end entity compx1;
11
12 architecture compx1 of compx1 is
13 begin
14     -- for the multiplexing of two hex input busses
15     A_less_B <= NOT bit_A AND bit_B; --when A is 0 and B is 1
16     A_equal_B <= (bit_A AND bit_B) OR (NOT(bit_A) AND NOT(bit_B)); --when A is 1 and B is 1 or when A is 0 and B is 0
17     A_more_B <= bit_A AND NOT bit_B; --when A is 1 and B is 0
18 end compx1;
19
20
21

```

## LogicalStep\_Lab3\_top

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.numeric_std.all;
4
5  entity LogicalStep_Lab3_top is port (
6      clk_in_50      : in std_logic;
7      pb             : in std_logic_vector(3 downto 0); -- pb(2) fdoor; pb(1) window; pb(0) bdoor
8      sw             : in std_logic_vector(7 downto 0); -- The switch inputs
9      leds           : out std_logic_vector(7 downto 0); -- for displaying the switch content
10     seg7_data       : out std_logic_vector(6 downto 0); -- 7-bit outputs to a 7-segment
11     seg7_char1      : out std_logic; -- seg7 digi selectors
12     seg7_char2      : out std_logic; -- seg7 digi selectors
13 );
14 end LogicalStep_Lab3_top;
15
16
-- Architecture
architecture Energy_Monitor of LogicalStep_Lab3_top is
-- Components Used
-- Component compx4
component compx4 port (
    a0, b0, a1, b1, a2, b2, a3, b3 : in std_logic; --a is the current temp, b is the desired temp
    a_more_b, a_equal_b, a_less_b : out std_logic --one-bit output based on 4 compx1
);
end component;
-- Component segment7_mux
component segment7_mux port (
    clk : in std_logic := '0';
    DIN2 : in std_logic_vector(6 downto 0);
    DIN1 : in std_logic_vector(6 downto 0);
    DOUT : out std_logic_vector(6 downto 0);
    DIG2 : out std_logic;
    DIG1 : out std_logic
);
end component;
-- Component SevenSegment
component SevenSegment port (
    hex : in std_logic_vector(3 downto 0); -- The 4 bit data to be displayed
    sevenseg : out std_logic_vector(6 downto 0) -- 7-bit outputs to a 7-segment
);
end component;
-- Component vacation_mux
component vacation_mux port (
    desired_temp : in std_logic_vector(3 downto 0);
    vacation_select : in std_logic;
    hex_out : out std_logic_vector(3 downto 0)
);
end component;
-- Create any signals, or temporary variables to be used
signal temp_led0 : std_logic; -- a more b i.e. current more desired; truth value for led0 (furnace on, below temp)
signal temp_led1 : std_logic; -- truth value for led1 (at temp)
signal temp_led2 : std_logic; -- a more b i.e. current more desired; truth value for led2 (ac on, below temp)
signal seg7_A : std_logic_vector(6 downto 0); -- left display
signal seg7_B : std_logic_vector(6 downto 0); -- right display
signal desired : std_logic_vector(3 downto 0); -- output of vacation mux
-- Here the circuit begins
begin
    leds(3) <= (temp_led0 OR temp_led2) AND (pb(2) AND pb(1) AND pb(0)); --blower status
    leds(2) <= temp_led0 AND (pb(2) AND pb(1) AND pb(0)); -- furnace status
    leds(1) <= temp_led1; --desired temp status
    leds(0) <= temp_led2 AND (pb(2) AND pb(1) AND pb(0)); -- ac status
    leds(4) <= NOT(pb(0)); -- flip switches for led values
    leds(5) <= NOT(pb(1));
    leds(6) <= NOT(pb(2));
    leds(7) <= NOT(pb(3));
    INST0: compx4 port map(sw(0), desired(0), sw(1), desired(1), sw(2), desired(2), sw(3), desired(3), temp_led2, temp_led1, temp_led0);
    INST1: SevenSegment port map(sw(3 downto 0), seg7_A);
    INST2: SevenSegment port map(desired, seg7_B);
    INST3: segment7_mux port map(clk_in_50, seg7_A, seg7_B, seg7_data, seg7_char1, seg7_char2);
    INST4: vacation_mux port map(sw(7 downto 4), pb(3), desired); -- mux to select between '0100' and switches
end Energy_Monitor;

```

## Compx4

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity compx4 is
5  port (
6      a0, b0, a1, b1, a2, b2, a3, b3 : in std_logic; --one-bit input (A, B)
7      a_more_b, a_equal_b, a_less_b : out std_logic --one-bit output based on 4 compx1
8  );
9
10 end entity compx4;
11
12 architecture compx4 of compx4 is
13
14     -- Components Used --
15     component compx1 port (
16         bit_A, bit_B : in std_logic; --one-bit input (A, B)
17         A_less_B, A_equal_B, A_more_B : out std_logic --one-bit output
18     );
19     end component;
20
21     -- Signals Created --
22     signal a0_more_b0 : std_logic;
23     signal a1_more_b1 : std_logic;
24     signal a2_more_b2 : std_logic;
25     signal a3_more_b3 : std_logic;
26     signal a0_equal_b0 : std_logic;
27     signal a1_equal_b1 : std_logic;
28     signal a2_equal_b2 : std_logic;
29     signal a3_equal_b3 : std_logic;
30     signal a0_less_b0 : std_logic;
31     signal a1_less_b1 : std_logic;
32     signal a2_less_b2 : std_logic;
33     signal a3_less_b3 : std_logic;
34
35     -- Circuit Begins --
36     begin
37
38     INST0: compx1 port map(a0, b0, a0_more_b0, a0_equal_b0, a0_less_b0);
39     INST1: compx1 port map(a1, b1, a1_more_b1, a1_equal_b1, a1_less_b1);
40     INST2: compx1 port map(a2, b2, a2_more_b2, a2_equal_b2, a2_less_b2);
41     INST3: compx1 port map(a3, b3, a3_more_b3, a3_equal_b3, a3_less_b3);
42
43
44     a_equal_b <= a0_equal_b0 AND a1_equal_b1 AND a2_equal_b2 AND a3_equal_b3;
45     a_more_b <= (a3_more_b3) OR
46                 (a3_equal_b3 AND a2_more_b2) OR
47                 (a3_equal_b3 AND a2_equal_b2 AND a1_more_b1) OR
48                 (a3_equal_b3 AND a2_equal_b2 AND a1_equal_b1 AND a0_more_b0);
49     a_less_b <= (a3_less_b3) OR
50                 (a3_equal_b3 AND a2_less_b2) OR
51                 (a3_equal_b3 AND a2_equal_b2 AND a1_less_b1) OR
52                 (a3_equal_b3 AND a2_equal_b2 AND a1_equal_b1 AND a0_less_b0);|
53
54 end compx4;
```

vacation\_mux

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  entity vacation_mux is
5  port (
6      desired_temp      : in std_logic_vector(3 downto 0);
7      vacation_select    : in std_logic;
8      hex_out           : out std_logic_vector(3 downto 0)
9  );
10
11  end entity vacation_mux;
12
13  architecture mux_logic of vacation_mux is
14  begin
15      with vacation_select select
16          hex_out <= "0100" when '0', --when pb3 is not pressed
17                      desired_temp when '1'; --when pb3 is pressed
18  end mux_logic;
```